

Trabalho Prático 3

24 de março de 2021 09:13


Exercise 1

- $s \leq a \oplus b \oplus cin$;
- $cout \leq (a \text{ and } b) \text{ or } (cin \text{ and } (a \text{ or } b))$;


Exercise 2

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity FullAdder is
    port(a, b, cin: in
std_logic;
        s, cout : out
std_logic);
end FullAdder;
architecture Behavioral of
FullAdder is
begin
    s <= a xor b xor cin;
    cout <= (a and b) or (cin
and(a or b));
end Behavioral;
```

Exercise 3

 

Exercise 4

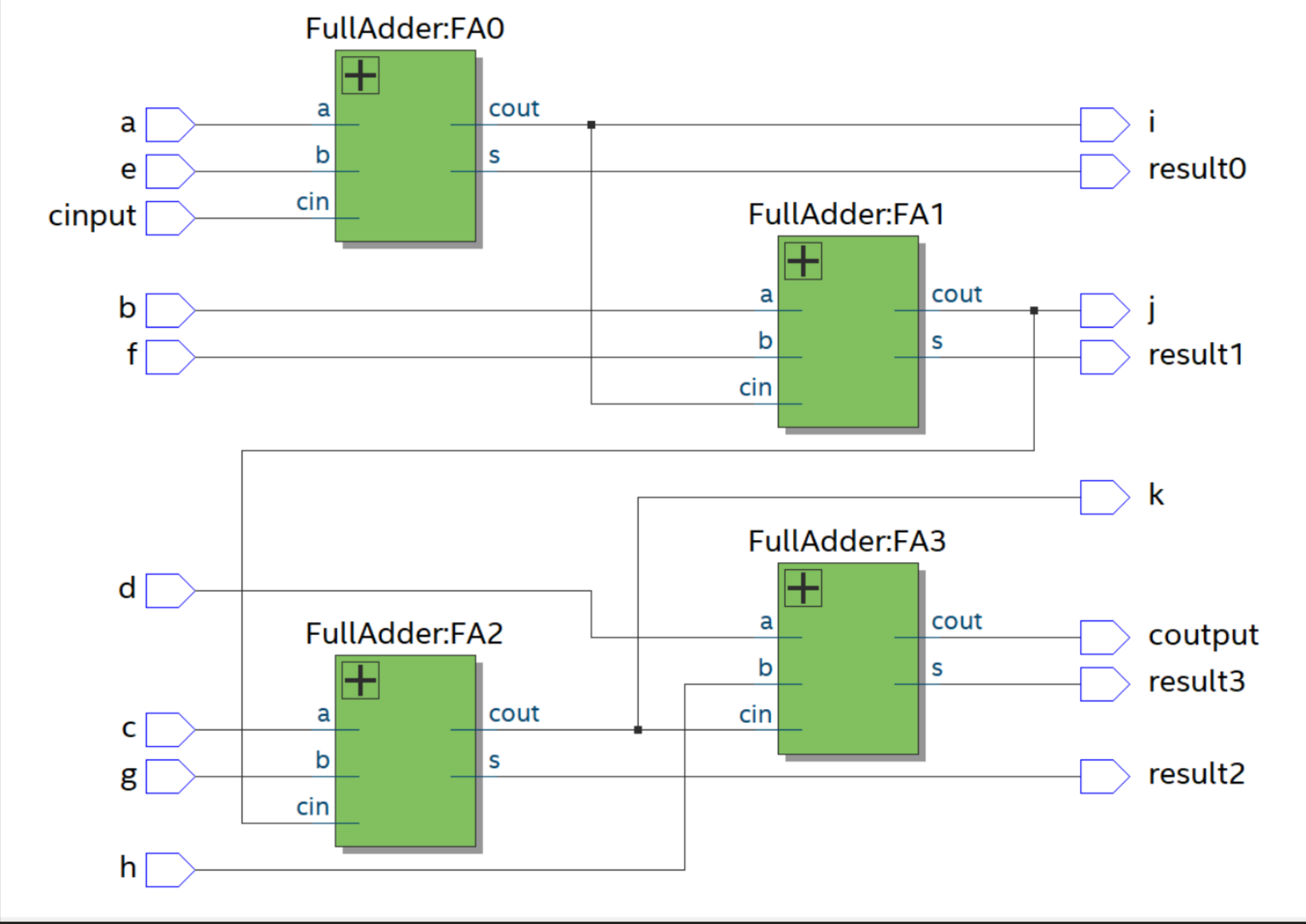


Exercise 5

Serão necessários 3 sinais de Carry (buffers i, j e k) para interligar os 4 full Adders de 1 bit, além disso existem ainda uma entrada Carry in (transporte de entrada) e uma saída Carry Out (transporte de saída).

Exercise 6

```
library IEEE;
use IEEE.STD_LOGIC_1164.all;
entity RippleCarry is
    port(a, e, b, f, c, g, d, h, cininput: in std_logic;
        i, j, k: buffer std_logic;
        result0, result1, result2, result3, cout: out std_logic);
end RippleCarry;
architecture Structural of RippleCarry is
begin
    FA0: entity work.FullAdder
        port map (a => a,
        b => e,
        cin=> cininput,
        s => result0,
        cout => i );
    FA1: entity work.FullAdder
        port map (a => b,
        b => f,
        cin=> i,
        s => result1,
        cout => j );
    FA2: entity work.FullAdder
        port map (a => c,
        b => g,
        cin=> j,
        s => result2,
        cout => k );
    FA3: entity work.FullAdder
        port map (a => d,
        b => h,
        cin=> k,
        s => result3,
        cout => cout );
end Structural;
```

Exercise 8

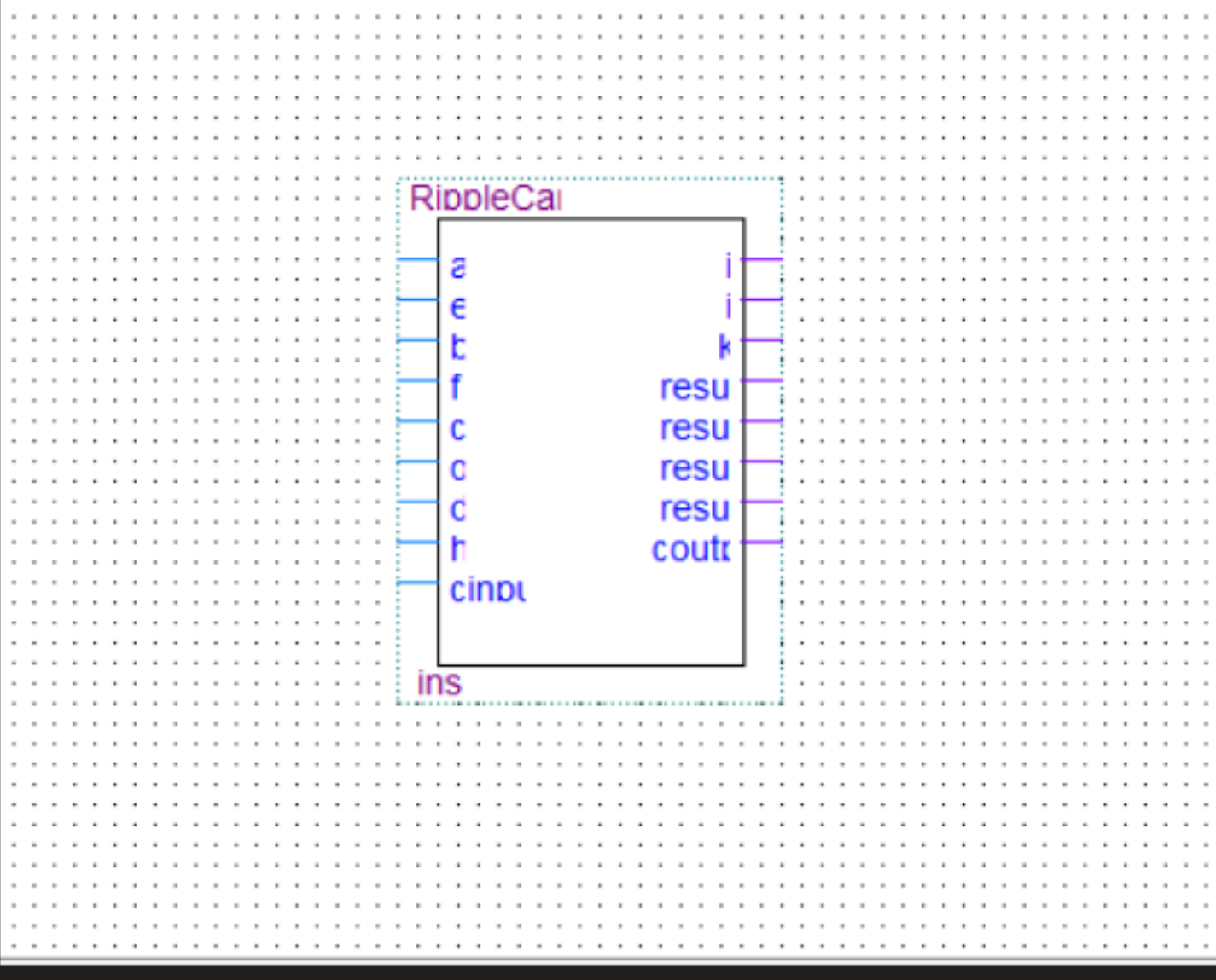

PARTE II

Exercise 1

- Adição - 1100
- Subtração - 0110
- Multiplicação - 11011
- Divisão - 0011
- AND - 0001
- OR - 1011
- XOR - 1010

Exercise 4

